


Tutorial 8

Name: Nour-alain Ibrahim Ahmed Elbadawy

ID: 2018-13394

 Q1)


Consider the state diagram of a sequential circuit is given as shown:




- Minimize the number of states with the aid of state table.
- Write the VHDL code to describe the minimized FSM.
- Implement the minimized FSM diagram using T- flip flops.
- Write a VHDL code to describe the circuit implemented in part (c).

Question 1:

Consider the state diagram of a s

 

State	next state		O/P
	x=0	x=1	
A	A	D	0
D	A	E	0
E	A	E	1

 

- Minimize the number
- Write the VHDL code
- Implement the minimi
- Write a VHDL code to

```

library ieee;
use ieee.std_logic_1164.all;

entity sheet5 is
    port(
        x,clk,rst:in std_logic;
        z: out std_logic
    );
end entity;

architecture behave of sheet5 is

    type states is (A,D,E);
    signal cs,ns : states;  --Current state, Next state

begin

    process (clk,rst)
    begin

        if rst='1' then cs <= A;

        elsif rising_edge (clk) then cs <= ns;

        end if;

    end process;

    process( clk, x )
    begin

        if cs = A then
            if x='0' then ns <= A;

            else ns <= D;

            end if;

        elsif cs = D then

```

```

        if x= '0' then ns <= A;

        else ns <= E;

        end if;

    elsif cs = E then
        if x= '0' then ns <= A;

        else ns <= E;

        end if;


    end if;

end process;

z <= '1' when cs = E else '0';

end behave;

```

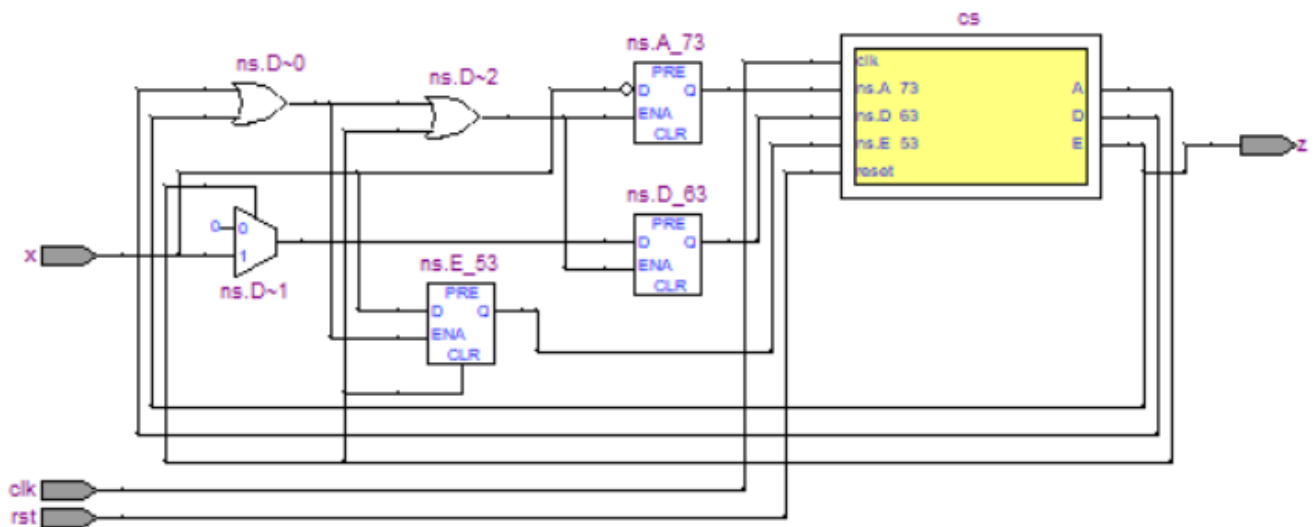

Current	Next (x=0)	Next (x=1)	Output
A	A	D	0
D	A	E	0
E	A	E	1

Current	I/P	Next	FF I/P	O/P
$Q_1 Q_2$	X	$Q_1^+ Q_2^+$	$T_1 T_2$	Z
00	0	00	00	0
00	1	01	01	0
01	0	00	01	0
01	1	10	11	0
10	0	00	10	1
10	1	10	00	1

$$Z = Q_1 \overline{Q_2}$$

$$T_1 = \overline{Q_1} Q_2 X + Q_1 \overline{Q_2} \overline{X}$$

$$T_2 = \overline{Q_1} \overline{Q_2} X + \overline{Q_1} Q_2$$

```

library ieee;
use ieee.std_logic_1164.all;

entity sheet5 is
    port(
        x,clk,rst:in std_logic;
        z: out std_logic
    );

```


```

end entity;

architecture behave of sheet5 is
    signal q1,q2,t1,t2: std_logic;
begin
    z <= q1 and not(q2);
    t1 <= (not(q1) and q2 and x) or (q1 and not(q2) and not(x));
    t2 <= (not(q1) and not(q2) and x) or (not(q1) and q2);


    process(rst,clk)
    begin
        if(rst='1') then
            q1 <= '0';
            q2 <= '0';
        elsif(rising_edge(clk)) then
            if(t1='1') then
                q1 <= not(q1);
            end if;
            if(t2='1') then
                q2 <= not(q2);
            end if;
        end if;
    end process;
end architecture;

```

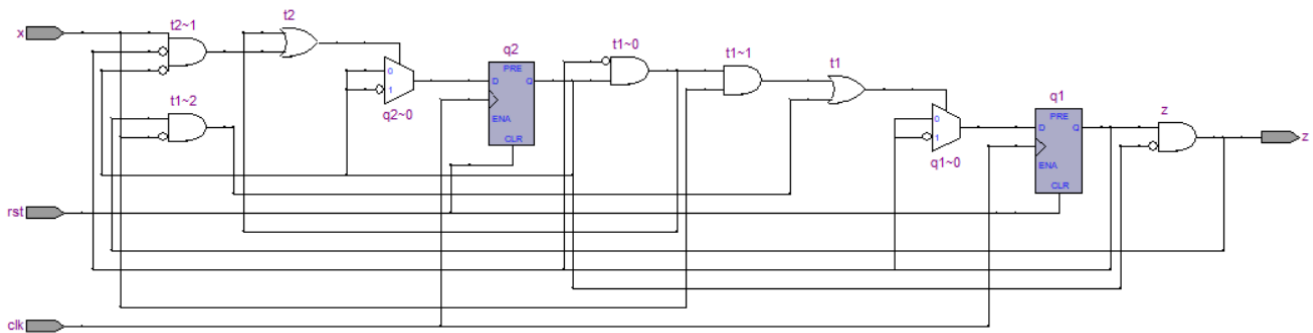


Q2)

Consider the FSM diagram Shown

 

 - Minimize the FSM, and draw the minimized FSM diagram.
- Write the VHDL code to describe the minimized FSM.
- Implement the minimized FSM using D-Flip flops, and make sure that your design is suitable for testability.



```

library ieee;
use ieee.std_logic_1164.all;

entity sheet5 is
    port(
        rst,clk,x1 : in std_logic;
        z : out std_logic
    );
end entity;

architecture behave of sheet5 is
    type states is (a,b,c,d,e);
    signal ps,ns: states;
begin
    process(rst,clk)
    begin
        if rst='1' then ps <= a;
        elsif rising_edge(clk) then ps <= ns;
    end process;
end architecture;

```

```

        end if;
    end process;


    process(clk,x1,ps)
    begin
        case ps is
            when a =>
                if x1='0' then
                    ns <= a;
                    z <= '0';
                else ns <= b;
                    z <= '0';
                end if;
            when b =>
                if x1='0' then
                    ns <= c;
                    z <= '0';
                else ns <= d;
                    z <= '0';
                end if;
            when c =>
                if x1='0' then
                    ns <= a;
                    z <= '0';
                else ns <= d;
                    z <= '0';
                end if;
            when d =>
                if x1='0' then
                    ns <= a;
                    z <= '0';
                else ns <= b;
                    z <= '0';
                end if;
            when e =>
                if x1='0' then
                    ns <= a;
                    z <= '0';
                else ns <= d;
                    z <= '1';
                end if;
        end case;
    end process;

```

```

end process;
end behave;

```

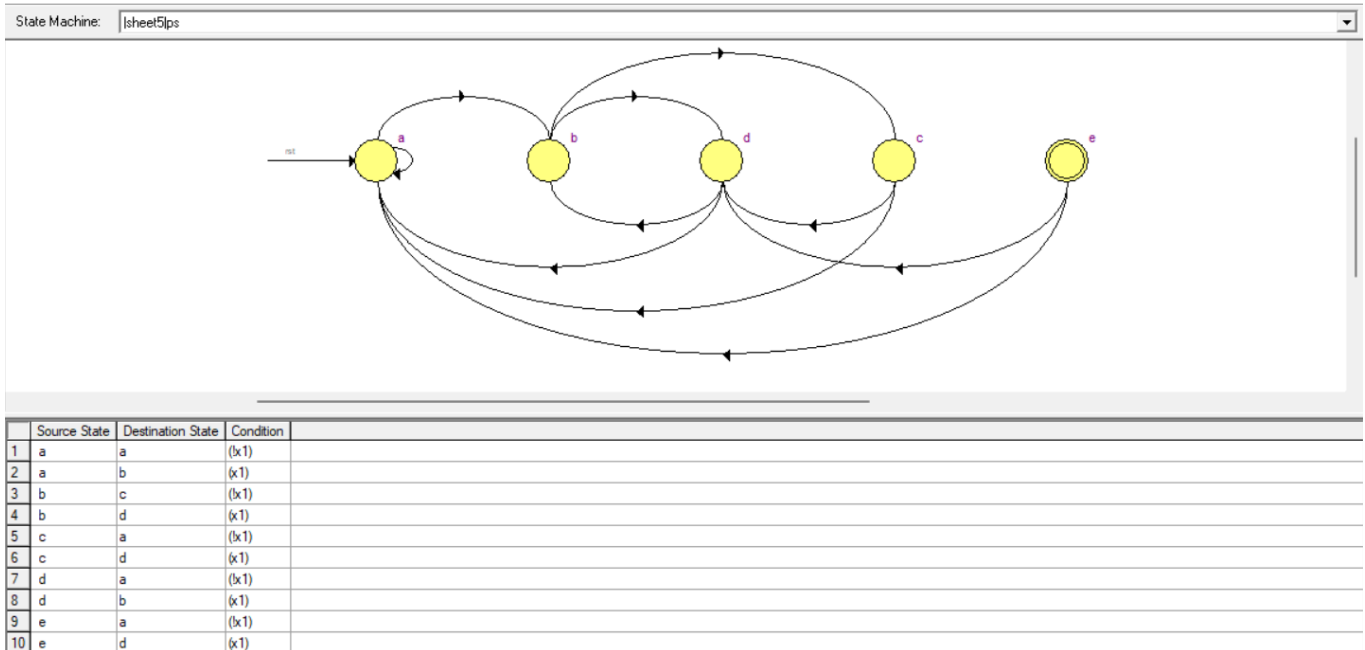

```

library ieee;
use ieee.std_logic_1164.all;

entity sheet5 is
    port(
        rst, clk, x1: in std_logic;
        z: out std_logic
    );
end entity;

architecture behave of sheet5 is
    type states is (a, b, c, d, e);
    signal ps, ns: states;

    signal d_a, d_b, d_c, d_d, d_e: std_logic;
    signal q_a, q_b, q_c, q_d, q_e: std_logic;
begin
    -- D flip-flop process for state a
    d_a <= '0' when x1 = '0' else '1';
    process(clk, rst)
    begin
        if rst = '1' then
            q_a <= '0';
        elsif rising_edge(clk) then

```

```

        q_a <= d_a;
    end if;
end process;

-- D flip-flop process for state b
d_b <= '0' when x1 = '0' else '0';
process(clk, rst)
begin
    if rst = '1' then
        q_b <= '0';
    elsif rising_edge(clk) then
        q_b <= d_b;
    end if;
end process;

-- D flip-flop process for state c
d_c <= '0' when x1 = '0' else '1';
process(clk, rst)
begin
    if rst = '1' then
        q_c <= '0';
    elsif rising_edge(clk) then
        q_c <= d_c;
    end if;
end process;

-- D flip-flop process for state d
d_d <= '0' when x1 = '0' else '0';
process(clk, rst)
begin
    if rst = '1' then
        q_d <= '0';
    elsif rising_edge(clk) then
        q_d <= d_d;
    end if;
end process;

-- D flip-flop process for state e
d_e <= '1' when x1 = '0' else '0';
process(clk, rst)
begin
    if rst = '1' then
        q_e <= '0';

```

```

        elsif rising_edge(clk) then
            q_e <= d_e;
        end if;
    end process;

    -- State transition process
    process(ps, q_a, q_b, q_c, q_d, q_e)
    begin
        case ps is
            when a =>
                ns <= b;
                z <= '0';
            when b =>
                if q_b = '1' then
                    ns <= c;
                    z <= '0';
                else
                    ns <= d;
                    z <= '0';
                end if;
            when c =>
                if q_c = '1' then
                    ns <= d;
                    z <= '0';
                else
                    ns <= a;
                    z <= '0';
                end if;
            when d =>
                if q_d = '1' then
                    ns <= b;
                    z <= '0';
                else
                    ns <= a;
                    z <= '0';
                end if;
            when e =>
                if q_e = '1' then
                    ns <= d;
                    z <= '1';
                else
                    ns <= a;
                    z <= '0';
                end if;
            end case;
        end process;
    end
end

```

```

                                end if;

                                end case;
                                end process;

                                -- Assign present state to output of corresponding flip-flop
                                ps <= a when q_a = '1' else
                                    b when q_b = '1' else
                                    c when q_c = '1' else
                                    d when q_d = '1' else
                                    e;

                                end behave;

```

