

# Assignment 2


Name: Nour-alain Ibrahim Ahmed Elbadawy

ID: 2018-13394

## Q5)
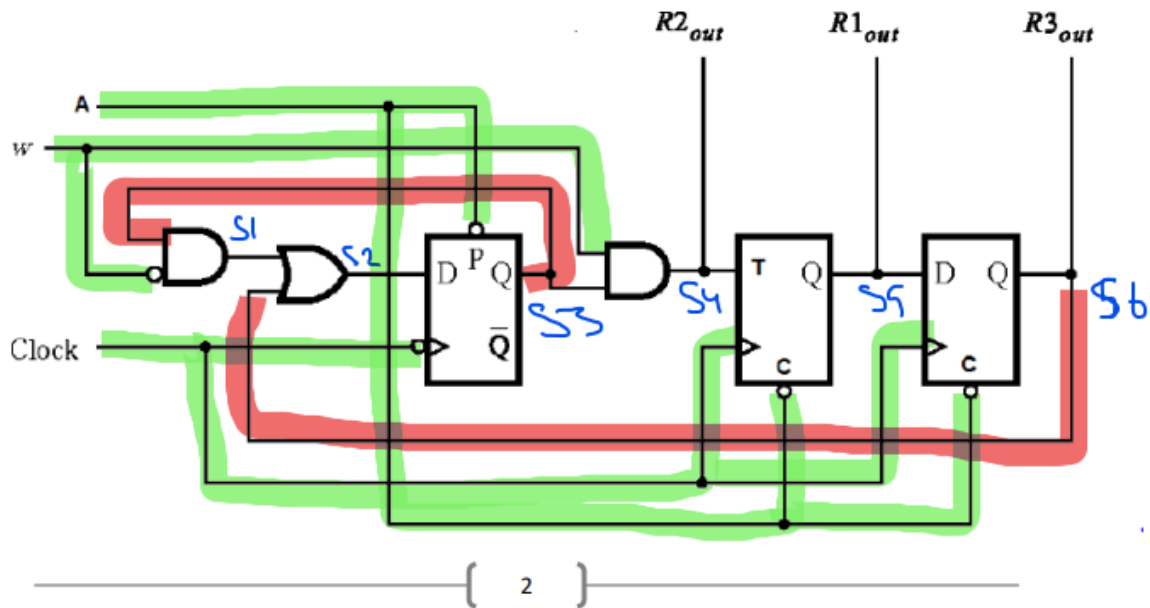
### Question 5: (Assignment)

Consider the circuit diagram shown in figure:



## Behavioral VHDL

### Main Code

```
library ieee;
use ieee.std_logic_1164.all;

entity Q5 is
port(
    a,w,clk : in std_logic;
    r1,r2,r3: out std_logic );
end entity;
```

```

architecture behave of Q5 is

    signal s1,s2,s3,s4,s5,s6: std_logic;

begin

    s1 <= not(w) and s3;
    s2 <= s6 or s1;

    process (clk,a)
    begin
        if ( falling_edge (clk) ) then
            if(a = '0') then
                s3 <= s2;
            end if;
        end if;
    end process;

    s4 <= s3 and w;
    r2 <= s4;

    process (clk,a)
    begin
        if ( rising_edge (clk) ) then
            if(a = '0') then
                s5 <= s4;
            end if;
        end if;
    end process;


    process (clk,a)
    begin
        if ( rising_edge (clk) ) then
            if(a = '0') then
                s6 <= s5;
            end if;
        end if;
    end process;

    r1 <= s5;
    r3 <= s6;

end behave;

```

# RTL

 

note that I didn't use D and T flip flop and I replaced them with register.

# Structural VHDL

## Main code

```
library ieee;
use ieee.std_logic_1164.all;

entity Q5 is
port(
    a,w,clk : in std_logic;
    r1,r2,r3: out std_logic );
end entity;

architecture behave of Q5 is

    signal s1,s2,s3,s4,s5,s6: std_logic;

    component DFF1 is
    port(
        p,d,clk : in std_logic;
        q : out std_logic
    );
    end component;

    component DFF2 is
    port(
        c,d,clk : in std_logic;
        q: out std_logic
    );
    end component;

    component TFF_1 is
    port(
        c,t,clk : in std_logic;
        q: out std_logic
    );
    end component;

begin
```

```
s1 <= not(w) and s3;  
s2 <= s6 or s1;
```

```
DFF_1: DFF1 port map( d => s2, q => s3, clk => clk, p => a);
```

```
s4 <= s3 and w;  
r2 <= s4;
```


```
TFF1: TFF_1 port map( c => a, t => s4, clk => clk, q => s5 );
```

```
DFF_2: DFF2 port map( d => s5, q => s6, clk => clk, c => a);
```

```
r1 <= s5;  
r3 <= s6;
```

```
end behave;
```

## RTL

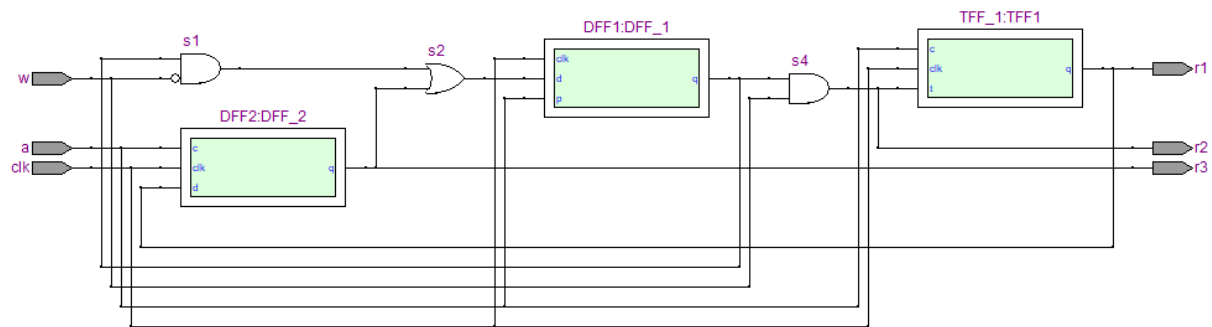

# TFF Component

```
library ieee;
use ieee.std_logic_1164.all;

entity TFF_1 is
port(
    c,t,clk : in std_logic;
    q: out std_logic );
end entity;

architecture behave of TFF_1 is

begin

q <= c and t and clk; -- just to get the rtl shape

end behave;
```

## DFF1 Component

```
library ieee;
use ieee.std_logic_1164.all;

entity DFF1 is
port(
    p,d,clk : in std_logic;
    q: out std_logic );
end entity;

architecture behave of DFF1 is

begin

q <= p and d and clk; -- just to get the rtl shape

end behave;
```

## DFF2 Component

```
library ieee;
use ieee.std_logic_1164.all;

entity DFF2 is
port(
    c,d,clk : in std_logic;
    q: out std_logic );
end entity;

architecture behave of DFF2 is

begin

q <= c and d and clk; -- just to get the rtl shape

end behave;
```