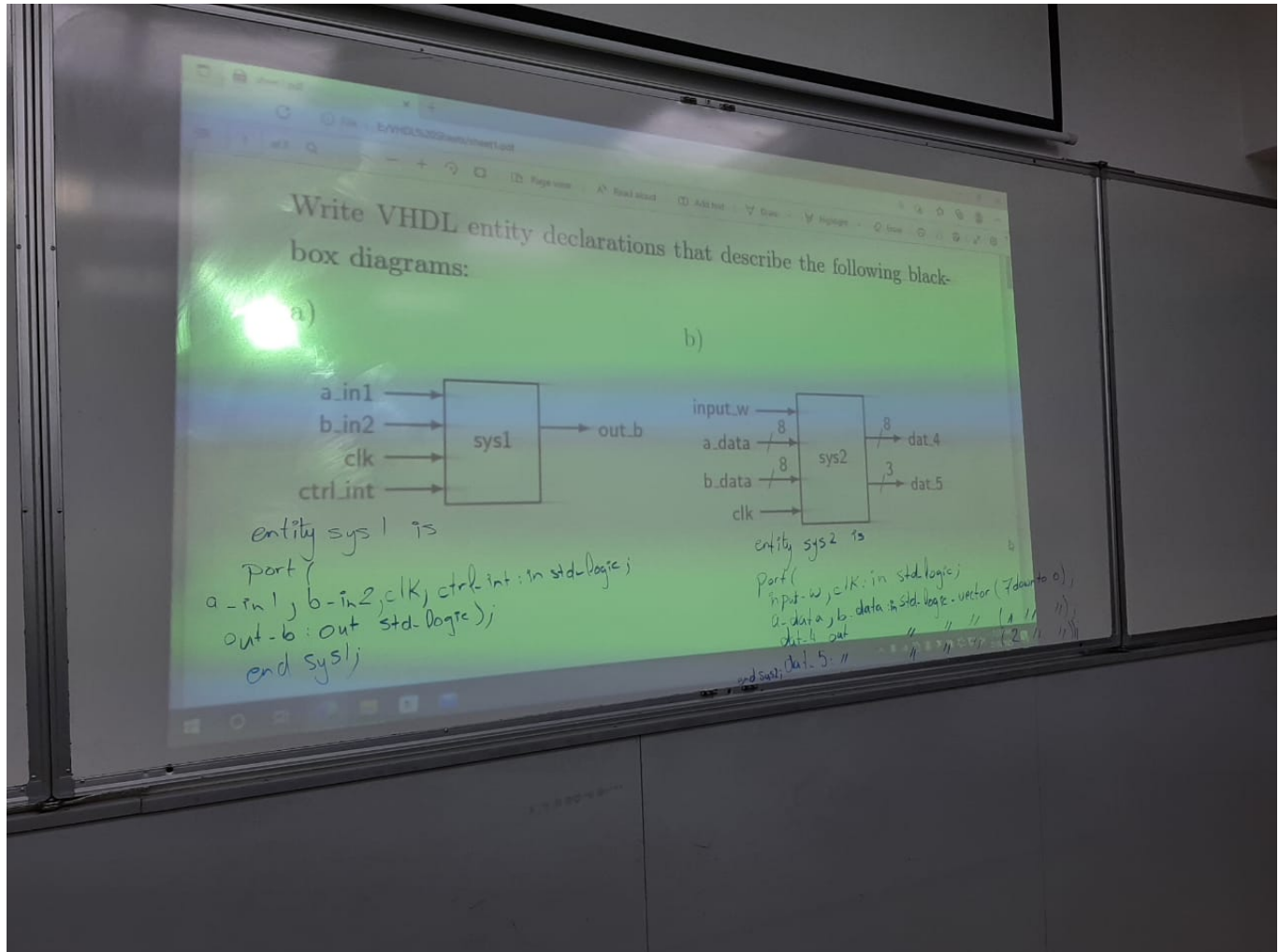


Tutorial 1

Name: Nour-alдин Ibrahim Ahmed Elbadawy

ID: 2018-13394

Q1)



a)


```
entity sys1 is
port(
a_in1, b_in2, clk, ctrl_int: in std_logic;
out_b: out std_logic
);
end sys1;
```

b)

```
entity sys2 is
port(
input_w, clk: in std_logic;
a_data, b_data: in std_logic_vector(7 downto 0);
dat_4: out std_logic_vector(7 downto 0);
dat_5: out std_logic_vector(2 downto 0)
);
end sys2;
```

Q2)


a)

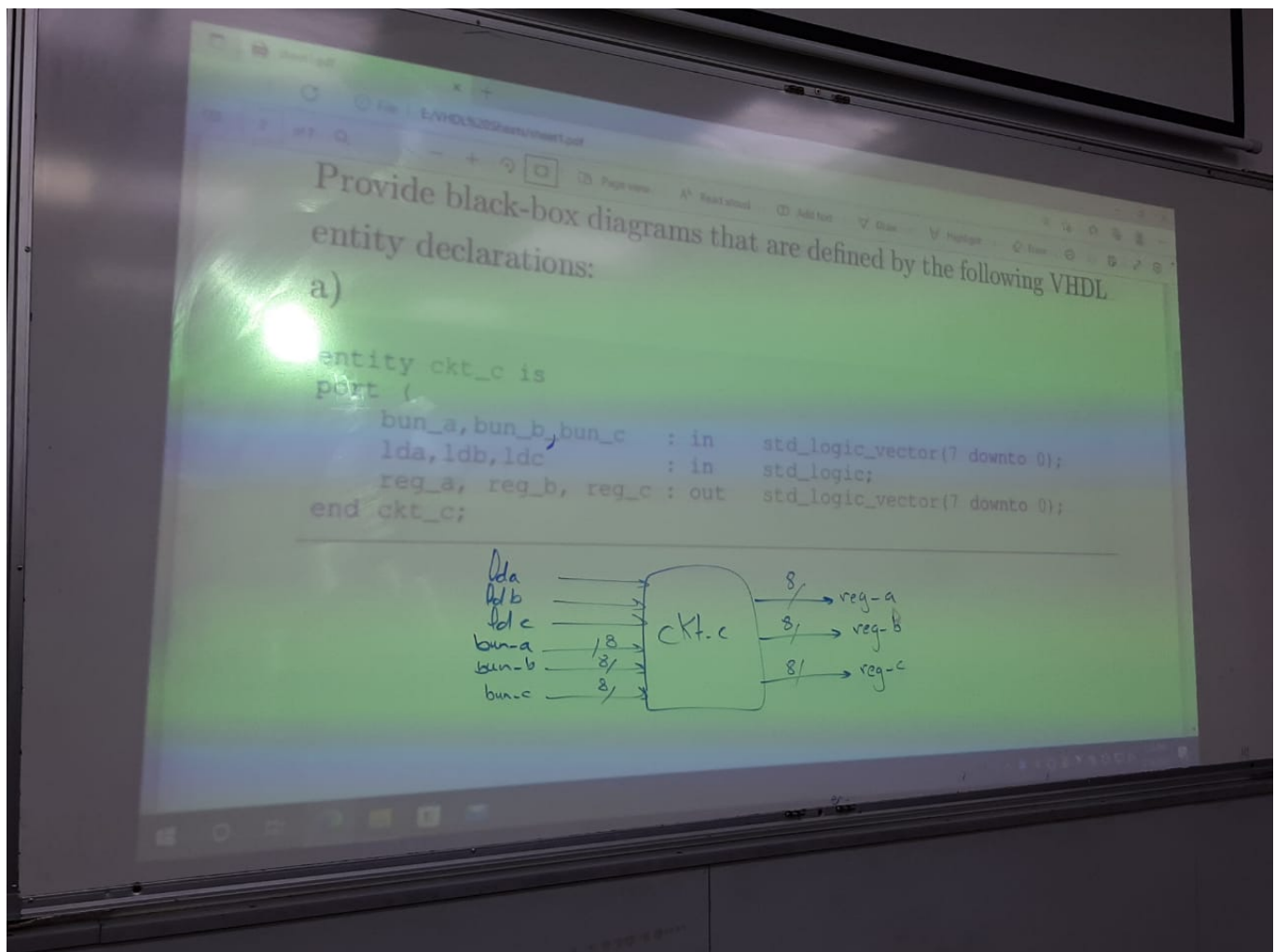

Q3)


Write VHDL entity declarations that describe the following block diagrams:

a)

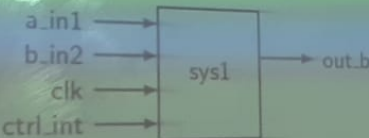

entity sys1 is
 port(
 a_in1, b_in2, clk, ctrl_int: in std_logic;
 out_b: out std_logic);
 end sys1;

b)

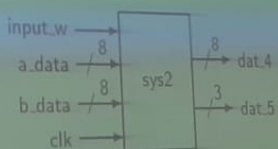

entity sys2 is
 port(
 input_w, clk: in std_logic;
 a_data, b_data: in std_logic_vector(7 downto 0);
 dat4: out std_logic_vector(7 downto 0);
 dat5: out std_logic_vector(2 downto 0));
 end sys2;

Q4)

a) $F(A,B) = !A B + A + A !B$


```
Library IEEE;  
use ieee.std_logic_1164.all;
```

```
entity tutorial1 is  
port(  
A,B: in std_logic;  
F: out Std_logic  
);  
end tutorial1;
```

```

architecture behave of tutorial1 is
begin
F <= ( (not A) and B) or (A) or (A and (not B) );
end architecture;

```

 

b) $F(A,B,C,D) = !A C !D + !B C + B C !D$


```

Library IEEE;
use ieee.std_logic_1164.all;

entity tutorial1 is
port(
A,B,C,D: in std_logic;
F: out Std_logic
);
end tutorial1;

architecture behave of tutorial1 is
signal x1, x2, x3: std_logic;
begin
x1 <= (not A) and C and (not D);
x2 <= (not B) and C;
x3 <= B and C and (not D);
F <= ( x1 ) or ( x2 ) or ( x3 );
end architecture;

```

 

c) $F(A,B,C,D) = (!A + B) \cdot (!B + C + !D) \cdot (!A + D)$


```

Library IEEE;
use ieee.std_logic_1164.all;


entity tutorial1 is
port(
A,B,C,D: in std_logic;
F: out Std_logic
);
end tutorial1;

architecture behave of tutorial1 is
signal x1, x2, x3: std_logic;
begin
x1 <= (not A) or B;
x2 <= (not B) or C or (not D);
x3 <= (not A) or D;
F <= ( x1 ) and ( x2 ) and ( x3 );
end architecture;

```

 

Q5)

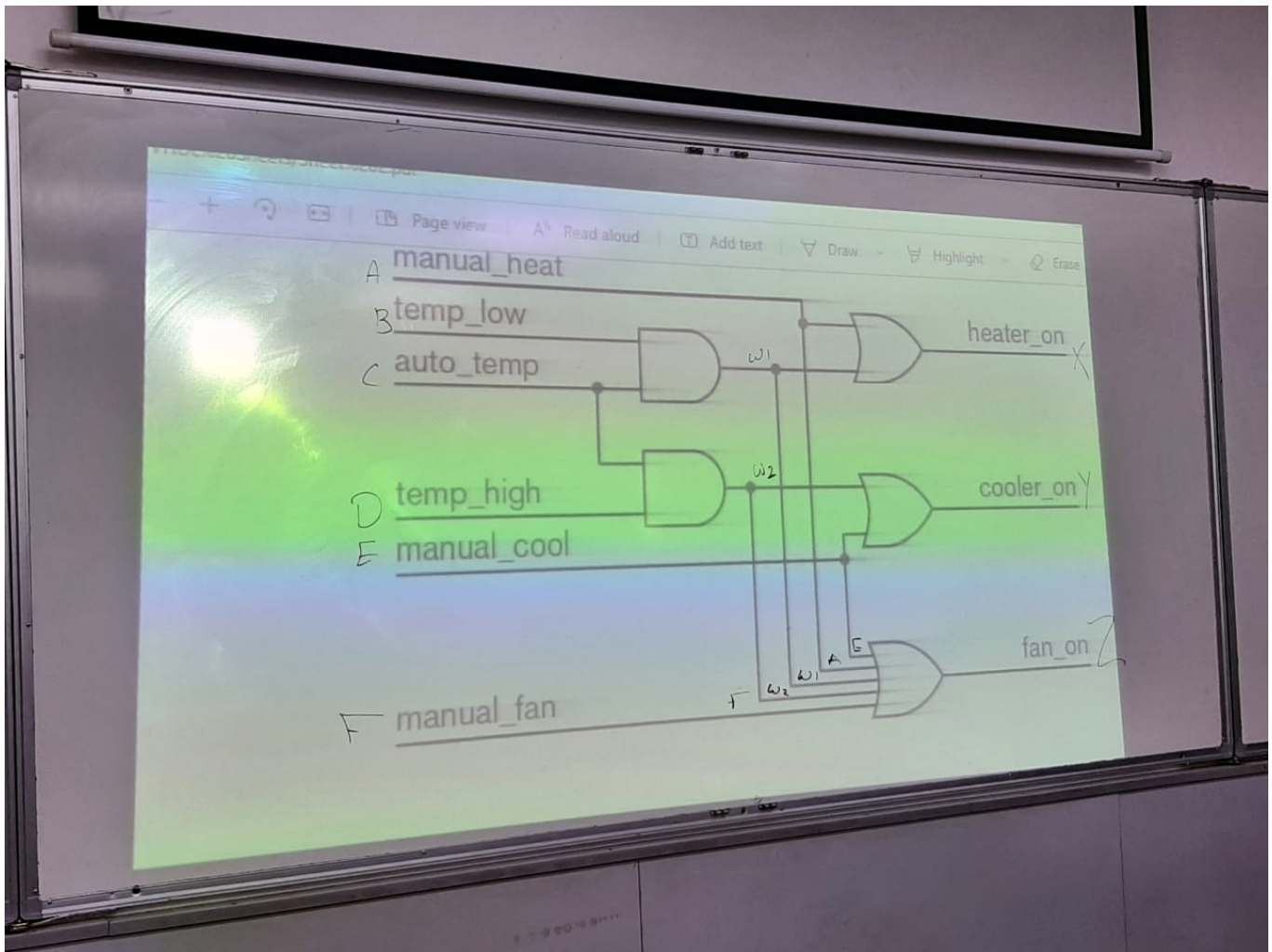

```

Library IEEE;
use ieee.std_logic_1164.all;

```

```

entity tutorial1 is
port(
A,B,C,D,E,F: in std_logic;
X,Y,Z: out Std_logic
);
end tutorial1;

architecture behave of tutorial1 is
signal w1, w2 : std_logic;
begin
w1 <= C and B;
w2 <= C and D;
X <= A or w1 ;
Y <= w2 or E;
Z <= E or A or w1 or w2 or F;
end architecture;

```

