

**Misr International University**  
**Electronics and Communication Engineering**  
**ECE 542 (VLSI Lab)**  
**Spring 2023**  
**Lab 3:**  
**NOR Gate**

**Dr. Ghazal Attia**  
**Eng. Habiba Mohamed**

Name	ID
Nour-Aldin Ibrahim Ahmed Azzab El-badawy	2018-13394

# Contents

Aim:.....	3
Introduction: .....	3
NOR Gate Schematic Design .....	4
NOR Gate Testbench.....	5
DC analysis .....	6
schematic: .....	6
simulation Output: .....	6
Transient Response analysis .....	7
schematic: .....	7
simulation Output: .....	8
NOR Gate Layout:.....	9
Testing.....	10
Design Rule Check Simulation ( DRC ):.....	10
Layout Versus Schematic ( LVS ) .....	10
Parasitic Extraction ( PEX ) .....	11
Post Layout Simulation .....	12
Conclusion:.....	13
Reference:.....	13

## Table of Figures:

Figure 1: NOR Schematic.....	3
Figure 2: NOR Truth Table.....	3
Figure 3: NOR Schematic.....	4
Figure 4: NOR Symbol .....	5
Figure 5: files of NOR testbench .....	5
Figure 6: DC analysis Schematic.....	6
Figure 7: DC analysis Output.....	6
Figure 8: Transient Analysis Schematic.....	7
Figure 9: Vpulse 1.....	7
Figure 10: Vpulse 2.....	7
Figure 11: Transient Analysis Simulation Output.....	8
Figure 12: NOR Layout .....	9
Figure 13: DRC.....	10
Figure 14: LVS.....	10
Figure 15 .....	11
Figure 16: Parasitic Components .....	11
Figure 17: Post Layout Simulation Output.....	12


## Aim:

The aim of this report is to explain the design process of a NOR gate using the Cadence tool. The design process consists of the following steps:

- Defining the specifications of the NOR gate
- Developing a behavioral model of the NOR gate
- Creating a schematic diagram of the NOR gate
- Testing the functionality and performance of the schematic design
- Designing a layout of the NOR gate
- Testing the layout design for any errors or violations
- Performing a post-layout simulation and verification
 
## Introduction:

A NOR gate is a basic logic gate that produces an output that is 0 if any of its inputs is 1, and 1 otherwise. For example, if the inputs are 0 and 1, the output is 0, and if the inputs are 0 and 0, the output is 1. NOR gates are widely used in digital circuits and systems, such as computers, calculators, and communication devices. In this report, we will describe how we designed a NOR gate using the Cadence tool, which is a software platform for electronic design automation. We will explain the steps we followed to create a schematic diagram, a layout design, and a post-layout simulation of the NOR gate. We will also present the results of our testing and verification of the design and discuss the challenges and limitations we faced during the design process.



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Figure 2: NOR Truth Table

 


Figure 1: NOR Schematic

## NOR Gate Schematic Design

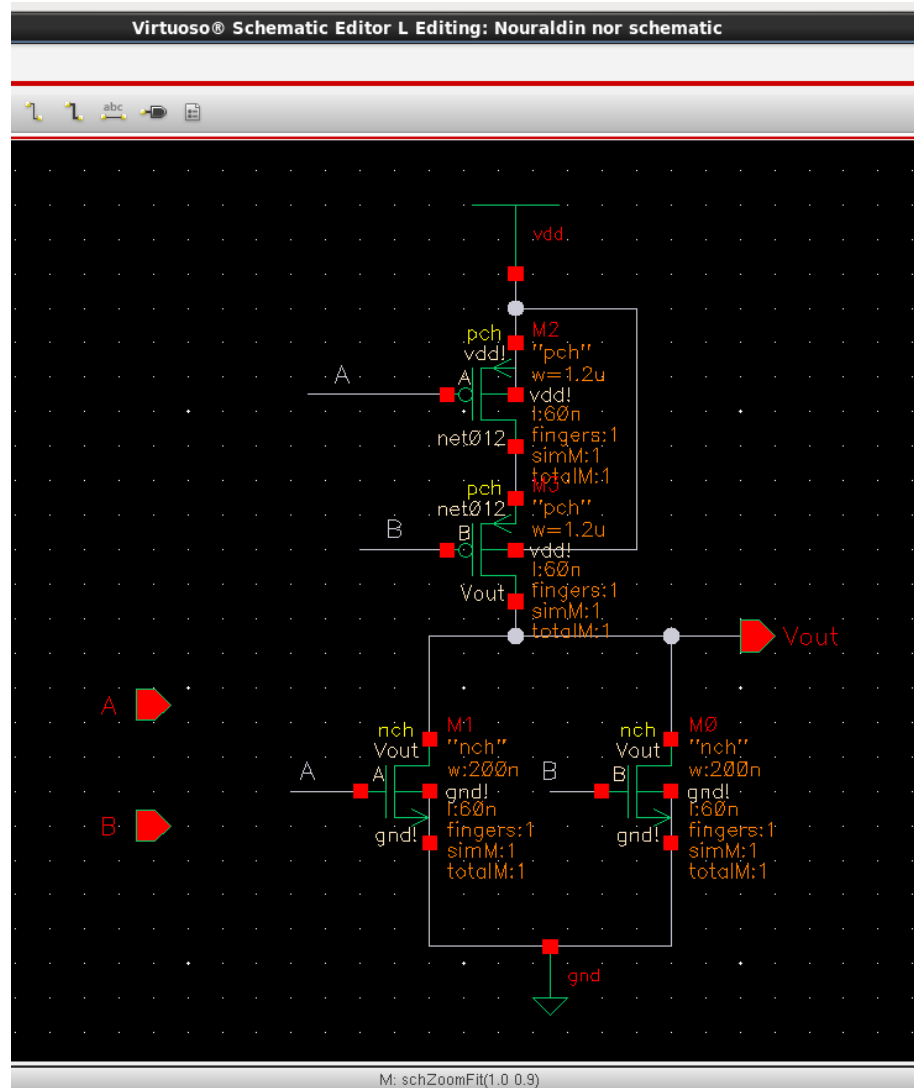


Figure 3: NOR Schematic

- The figure above shows the circuit schematic
- The circuit consists of:
  - Two PMOS transistors with  $L = 60\text{nm}$  and  $W = 1.2\mu\text{m}$
  - Two NMOS transistors with  $L = 60\text{nm}$  and  $W = 200\text{nm}$
- The inputs A and B are connected to:
  - The gate terminals of one PMOS and one NMOS transistor each

## NOR Gate Testbench

- We need to create a cell view

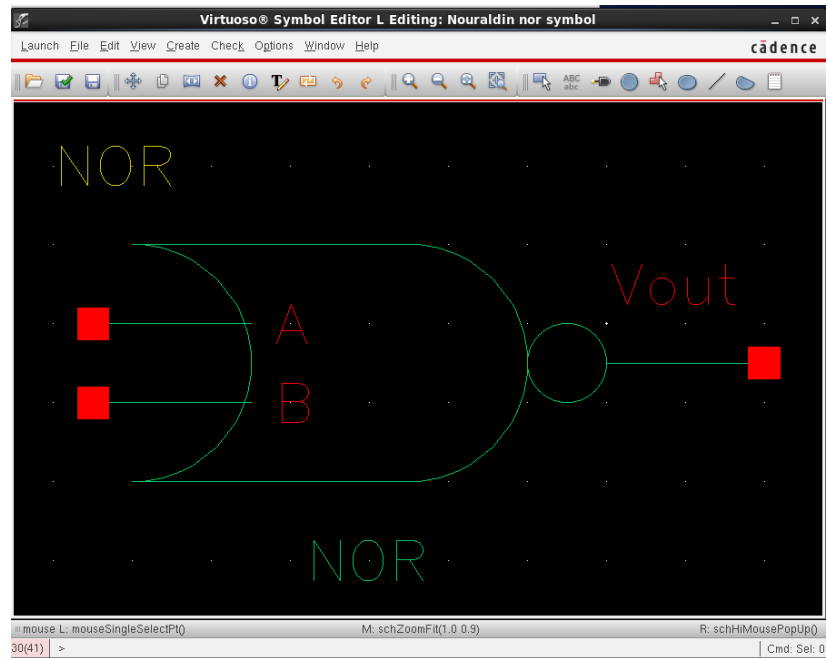


Figure 4: NOR Symbol

- Then we create a new cell called “NOR\_TB\_DC” for DC analysis and “NOR\_TB\_trans” for transient analysis.

```
nor_TB_DC
nor
nor_TB_DC
nor_TB_trans
```

Figure 5: files of NOR testbench

schematic:

We used a DC voltage source with value =  $v_b$  as an input.

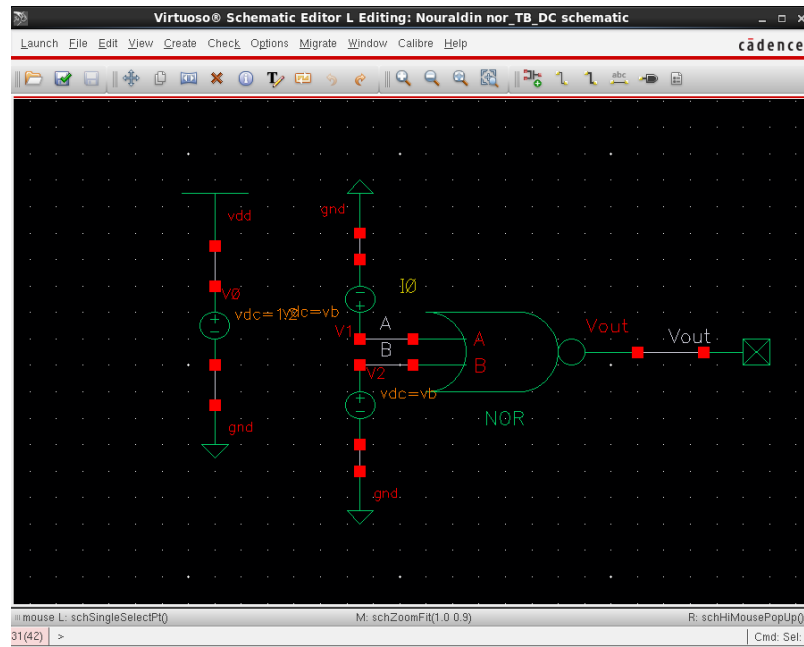


Figure 6: DC analysis Schematic

simulation Output:

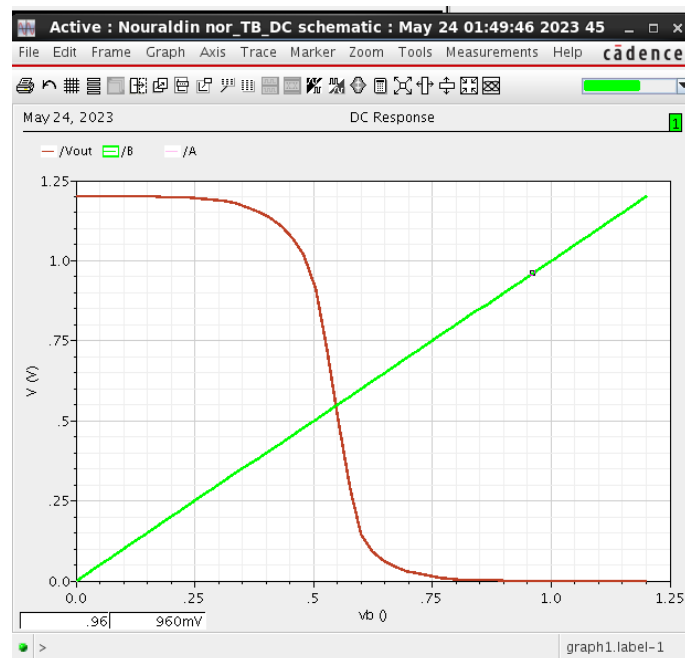


Figure 7: DC analysis Output

## Transient Response analysis

schematic:

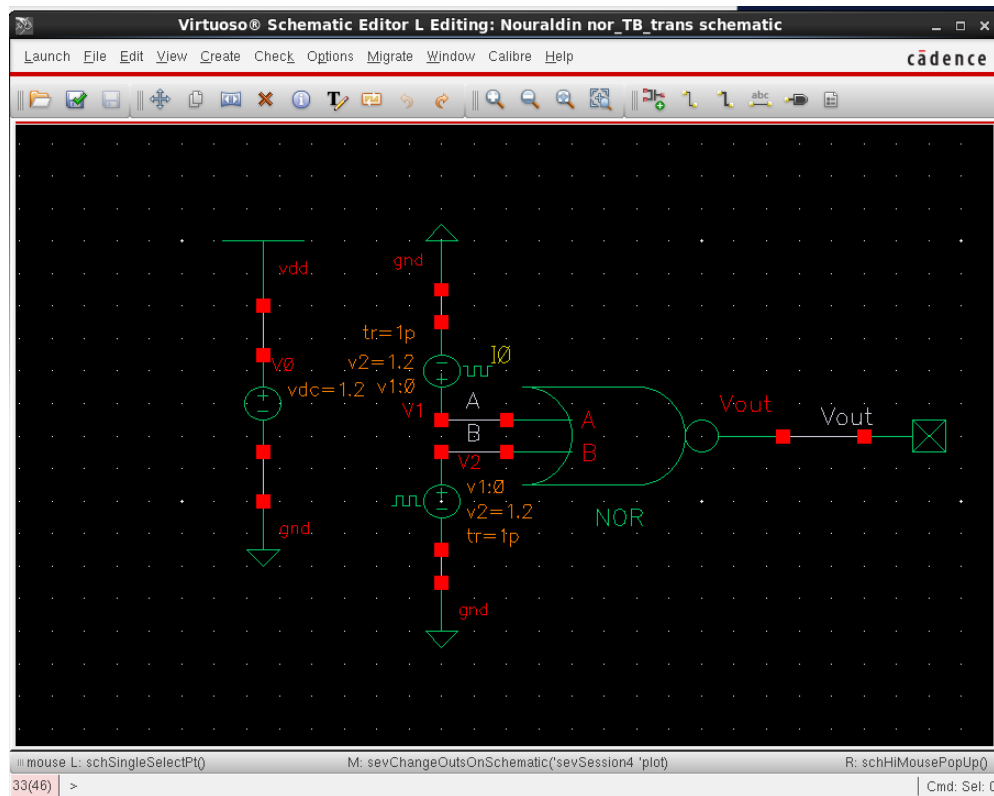


Figure 8: Transient Analysis Schematic

Vpulse voltage source was used to provide the input signal.

PAC magnitude		off
PAC phase		off
Voltage 1	0 V	off
Voltage 2	1.2 V	off
Period	200n s	off
Delay time	0 s	off
Rise time	1p s	off
Fall time	1p s	off
Pulse width	100n s	off
Temperature coefficient 1		off

Figure 9: Vpulse 1

PAC magnitude		off
PAC phase		off
Voltage 1	0 V	off
Voltage 2	1.2 V	off
Period	100n s	off
Delay time	0 s	off
Rise time	1p s	off
Fall time	1p s	off
Pulse width	50n s	off
Temperature coefficient 1		off
Temperature coefficient 2		off

Figure 10: Vpulse 2



### simulation Output:

The simulation shows that the output is 1 when Both A and B are 0, which confirms the correct functioning of the NOR.

 


Figure 11: Transient Analysis Simulation Output

## NOR Gate Layout:

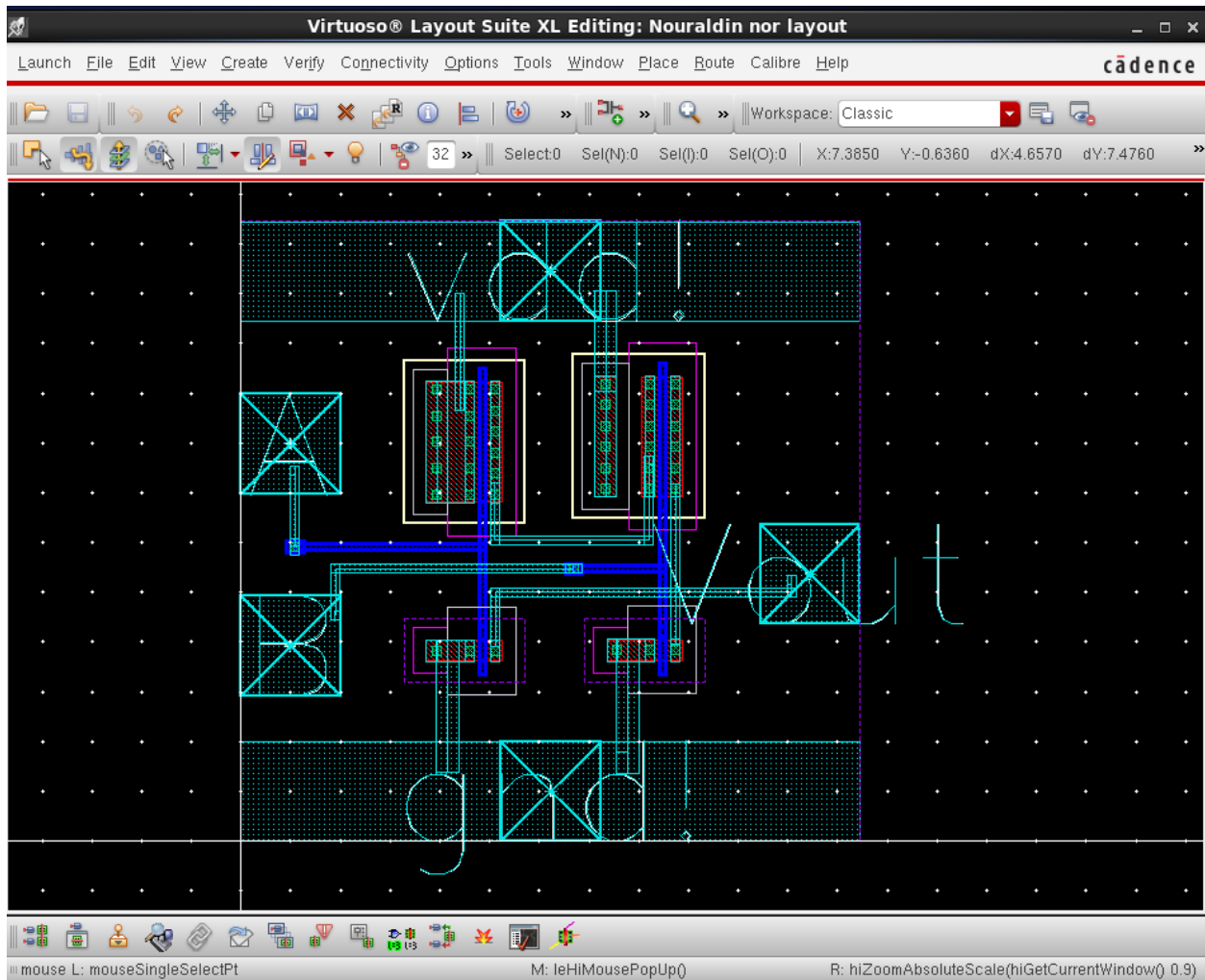


Figure 12: NOR Layout

## Testing

### Design Rule Check Simulation ( DRC ):

There is No Mx.S or A or W.

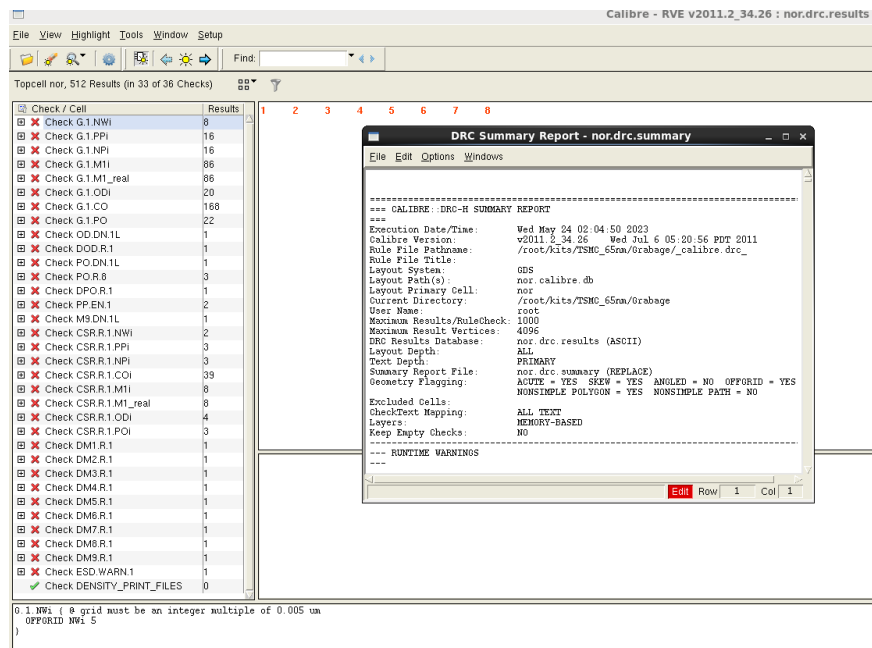


Figure 13: DRC

### Layout Versus Schematic ( LVS )

We have the smiley face 😊

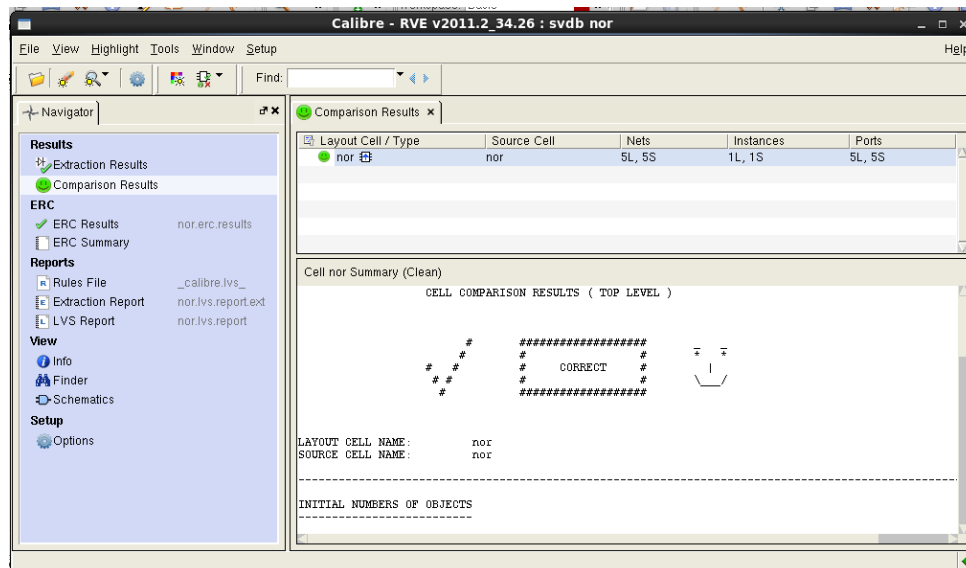


Figure 14: LVS

## Parasitic Extraction ( PEX )

Parasitic Extraction (PEX) is a process of calculating the unwanted effects of parasitic components, such as resistances, capacitances, and inductances, in an electronic circuit. PEX is used to create an accurate model of the circuit for simulation and verification purposes.

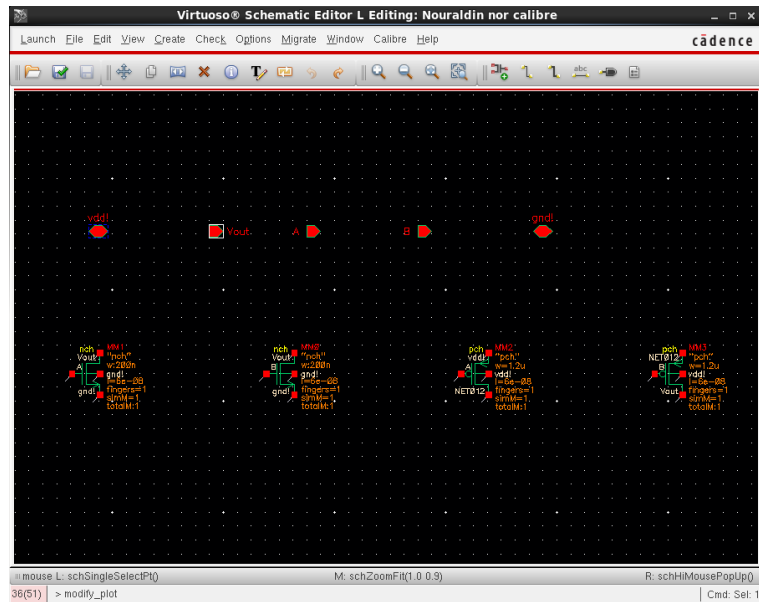


Figure 15

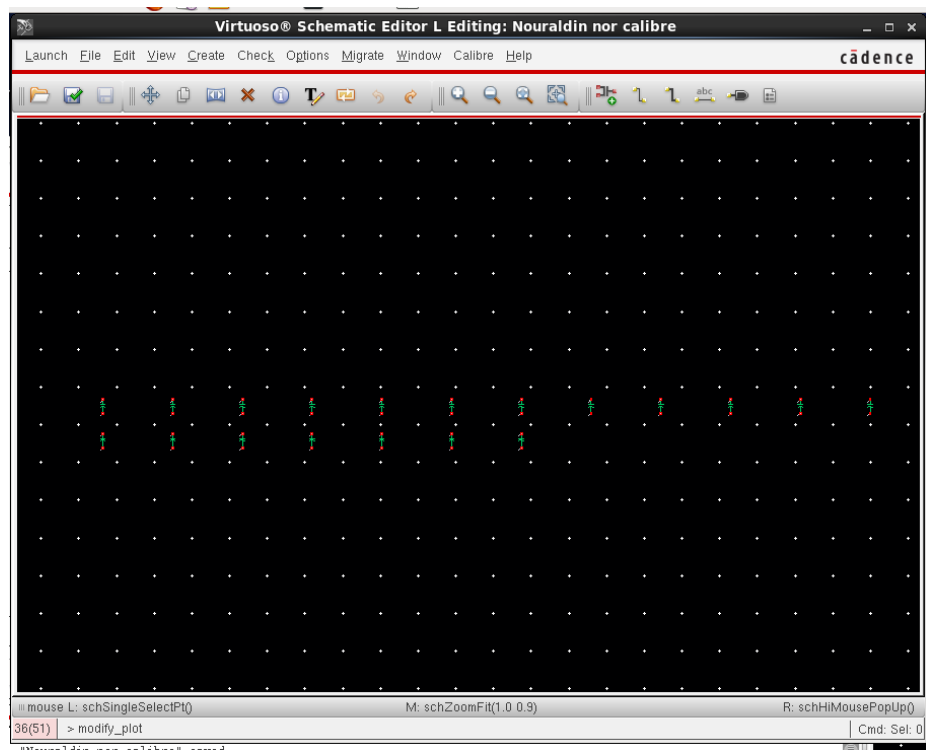


Figure 16: Parasitic Components

## Post Layout Simulation

The delay, which is 4.281ps as seen in the following figure, is within the acceptable range.

 


Figure 17: Post Layout Simulation Output

## Conclusion:

In this report, we have presented the design process of an NOR gate using the Cadence tool. We have successfully completed the following steps:

- Defined the specifications of the NOR gate
- Created a schematic diagram of the NOR gate
- Tested the functionality and performance of the schematic design
- Designed a layout of the NOR gate
- Tested the layout design for any errors or violations
- Performed a post-layout simulation and verification

We have demonstrated that our design meets the requirements and specifications of an NOR gate. We have also learned how to use the Cadence tool for electronic design automation, and gained valuable experience and skills in digital circuit design. We have encountered some challenges and limitations during the design process, such as choosing the appropriate parameters, optimizing the layout area, and ensuring the reliability and robustness of the design. We have overcome these challenges by applying the relevant concepts, methods, and tools that we have learned in this course. We hope that this report has provided a clear and comprehensive overview of our design process and results.

## Reference:

All the references are from the lab manual and from the Lecture by Dr. Ghazal Attia and Eng. Habiba Mohamed