

Tutorial 5

Name: Nour-alain Ibrahim Ahmed Elbadawy

ID: 2018-13394

full adder

code

```
-- Full Adder in VHDL
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity c_adder is
    Port ( num1 : in  STD_LOGIC_vector(3 downto 0);
          num2 : in  STD_LOGIC_vector(3 downto 0);
          Sum  : out STD_LOGIC_vector(3 downto 0);
          carry : out STD_LOGIC);
end c_adder;

architecture Behavioral of c_adder is

    signal c0,c1,c2,c3 : std_logic := '0';

begin
    -- first full adder
    Sum(0) <= num1(0) XOR num2(0); --sum calculation
    c0 <= num1(0) and num2(0); --carry calculation

    -- second full adder
    Sum(1) <= num1(1) XOR num2(1) XOR c0; --sum calculation
    c1 <= (num1(1) and num2(1) ) or (num1(1) and c0) or ( num2(1) and c0); --carry
    calculation

    -- third full adder
    Sum(2) <= num1(2) XOR num2(2) XOR c1; --sum calculation
    c2 <= (num1(2) and num2(2) ) or (num1(2) and c1) or ( num2(2) and c1); --carry
    calculation

    -- fourth full adder
    Sum(3) <= num1(3) XOR num2(3) XOR c2; --sum calculation
    c3 <= (num1(3) and num2(3) ) or (num1(3) and c2) or ( num2(3) and c2); --carry
```


calculation

```
-- final carry assignment
```


```
Carry <= c3;
```

```
end Behavioral;
```

RTL

 

Waveform

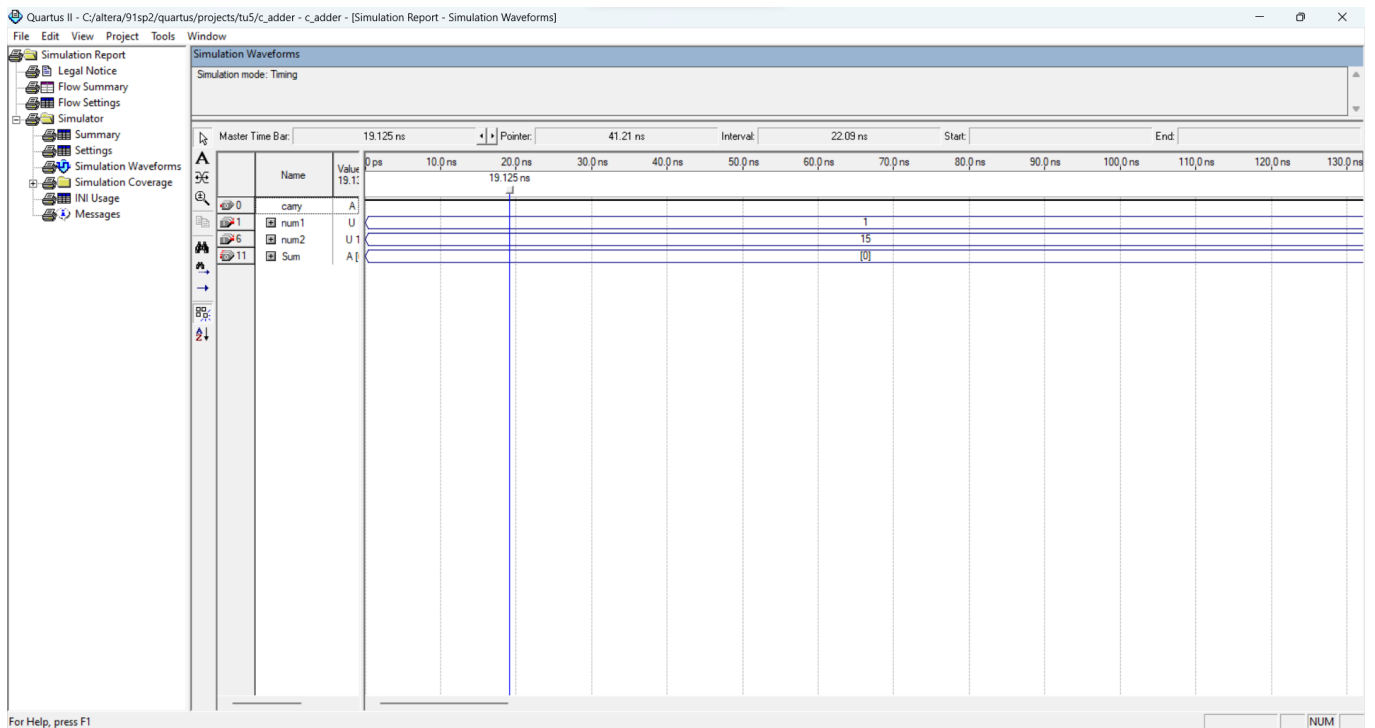

- .
- .
- .
- .
- .
- .

Multiplication

code

```
-- Multiplication in VHDL

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multi is
    Port ( a : in  STD_LOGIC_vector(3 downto 0);
          b : in  STD_LOGIC_vector(3 downto 0);
          output1 : out  STD_LOGIC_vector(7 downto 0)
        );
end multi;

architecture Behavioral of multi is


    signal ua: unsigned ( 3 downto 0);
    signal ub: unsigned ( 3 downto 0);
    signal uc: unsigned ( 7 downto 0);

begin

    --unsigned multiplication
    ua <= unsigned(a);
    ub <= unsigned(b);
    uc <= ua * ub;
    output1 <= std_logic_vector(uc);

end Behavioral;
```

RTL

 

Waveform

