


Tutorial 3

Name: Nour-alдин Ibrahim Ahmed Elbadawy


ID: 2018-13394

AND gate

 
```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity tu3 is  
port(  
    a,b : in std_logic;  
    c : out std_logic  
);  
  
end tu3;  
  
architecture behave of tu3 is  
  
begin  
  
    c <= a and b;  
  
end behave;
```



simulation mood: functional

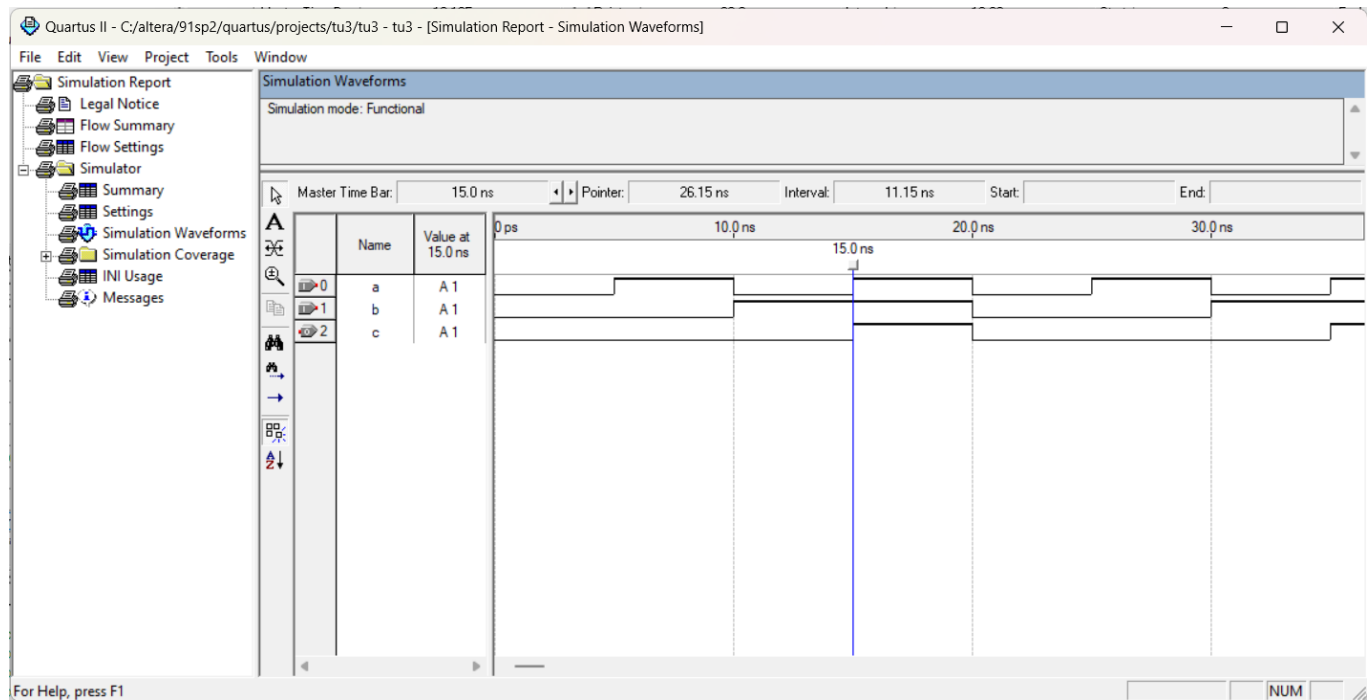


simulation mood: timing

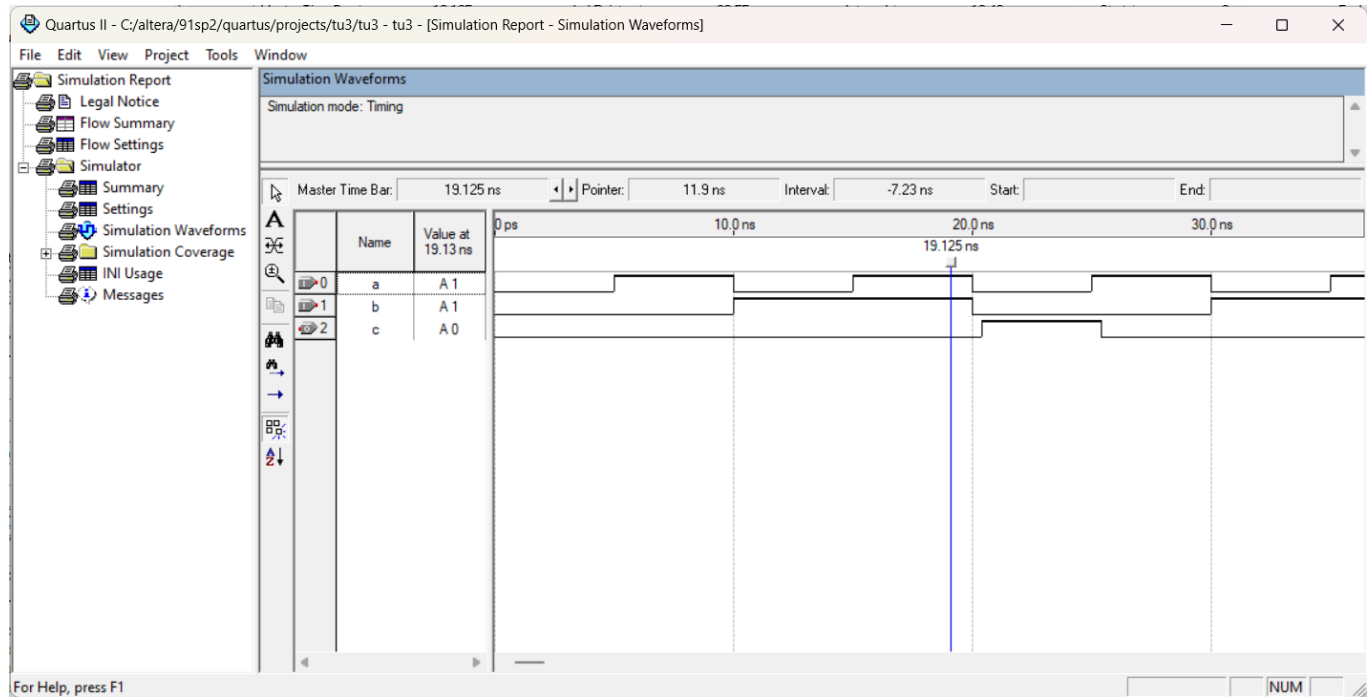


- .
- .
- .
- .
- .
- .
- .

OR gate

 
```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity tu3 is  
port(  
    a,b : in std_logic;  
    c : out std_logic  
);  
  
end tu3;  
  
architecture behave of tu3 is  
  
begin  
  
c <= a or b;  
  
end behave;
```



simulation mood: timing

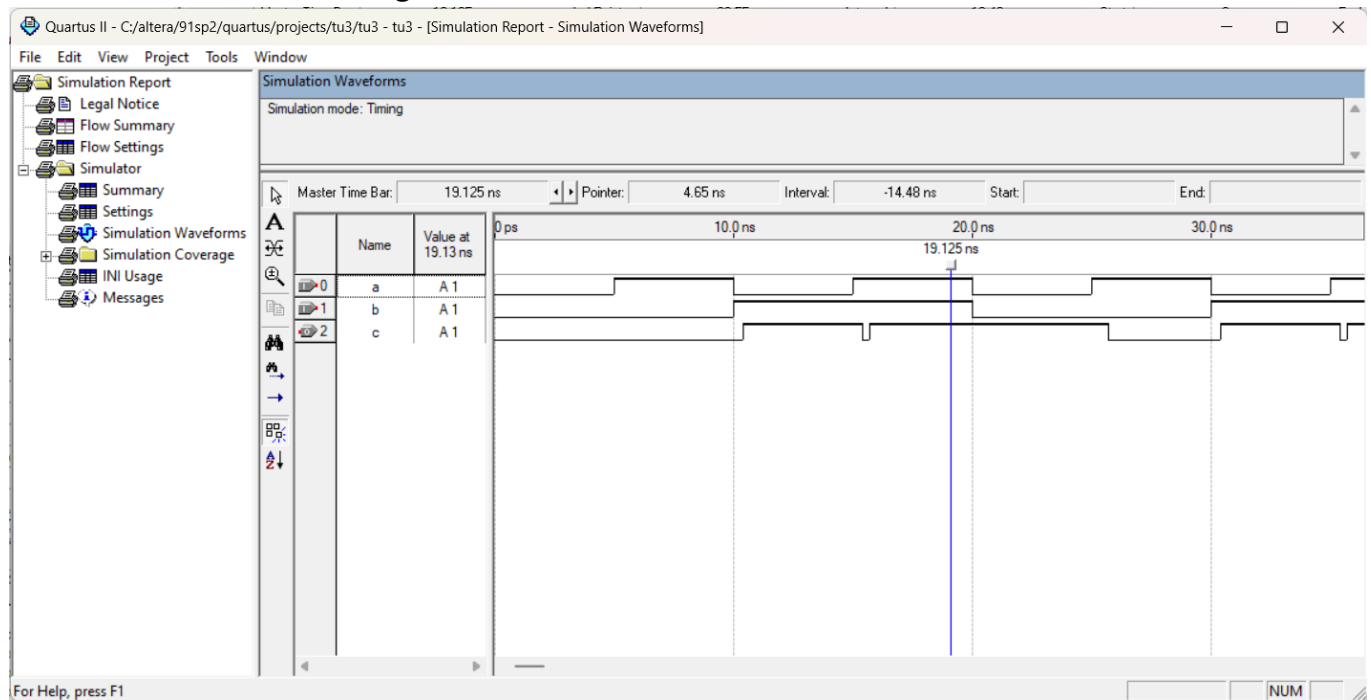

simulation mood: functional

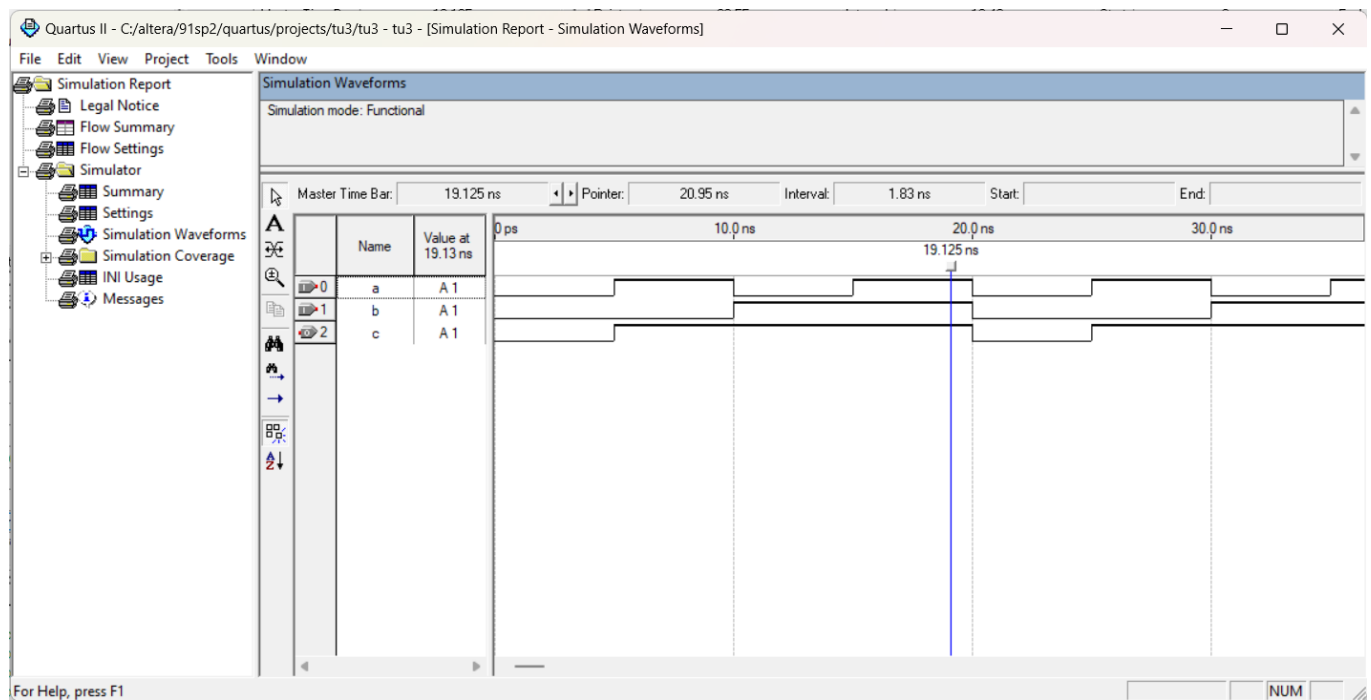



-
-
-
-
-

7 segment

```
library ieee;
use ieee.std_logic_1164.all;
entity tu3 is
port(
    d_in : in std_logic_vector(3 downto 0);
    d_out : out std_logic_vector(6 downto 0) );
end tu3;

architecture behave of tu3 is
begin
    process (d_in)
    begin
        case d_in is
            when "0000" => --0
                d_out <= "1111110";
            when "0001" => --1
                d_out <= "0110000";
            when "0010" => --2
                d_out <= "1101101";
            when "0011" => --3
                d_out <= "1111001";
            when "0100" => --4
                d_out <= "0110011";
            when "0101" => --5
                d_out <= "1011011";
            when "0110" => --6
                d_out <= "1011111";
            when "0111" => --7
                d_out <= "1110000";
            when "1000" => --8
                d_out <= "1111111";
            when "1001" => --9
                d_out <= "1111011";
            when others =>
                d_out <= "1001111";
        end case;
    end process;
end behave;
```

simulation mood: functional

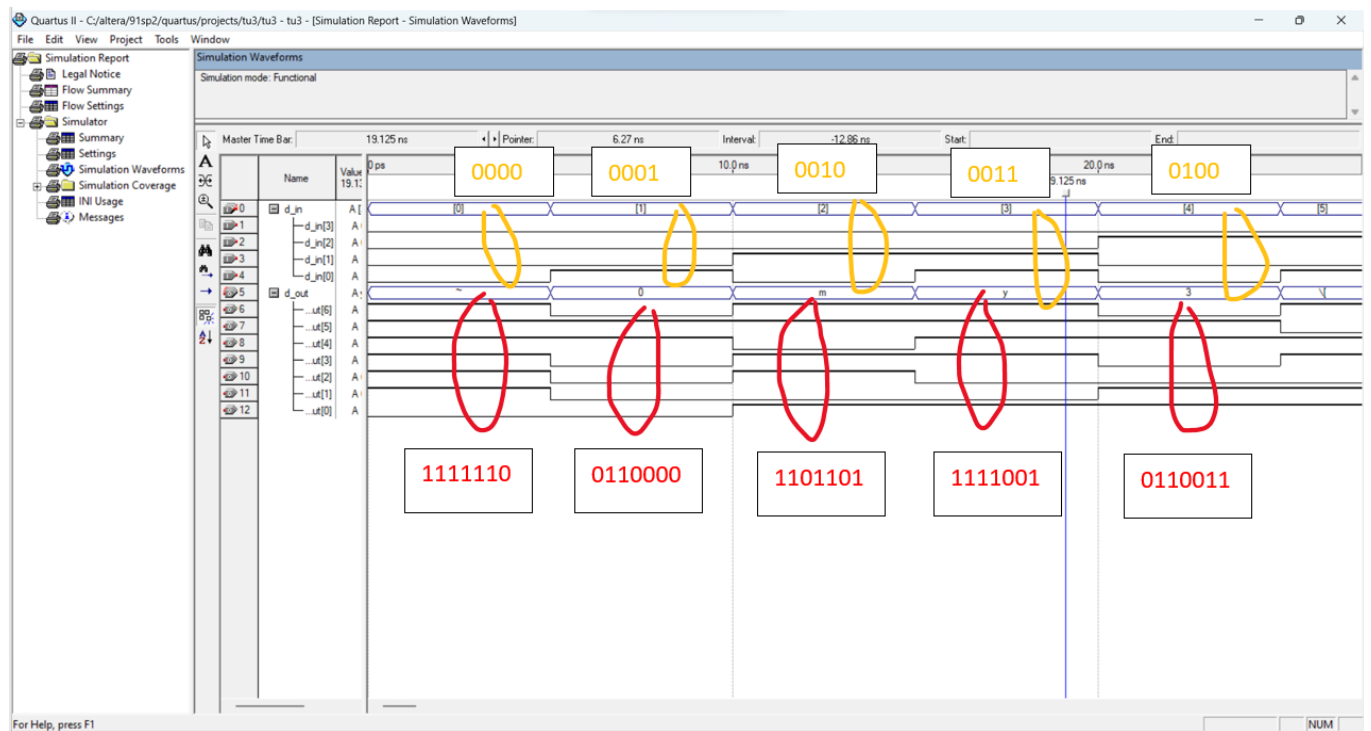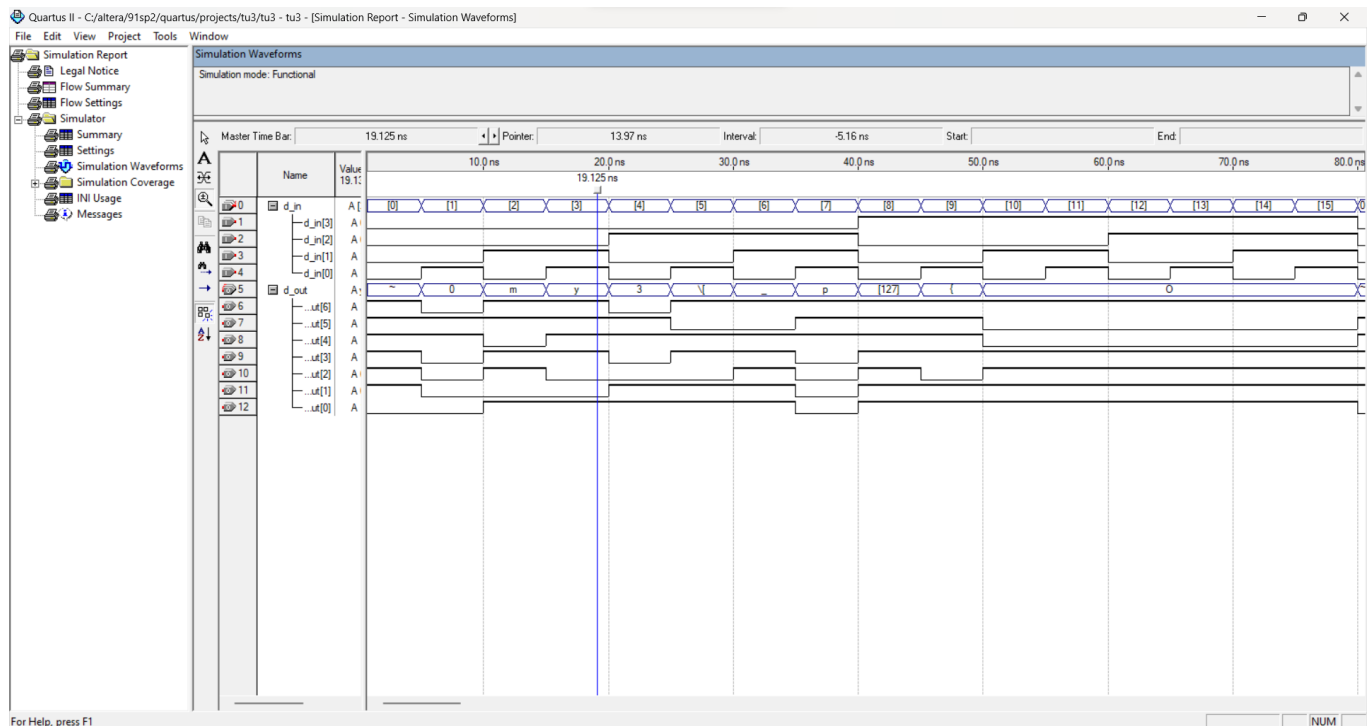


MUX


```
library ieee;
use ieee.std_logic_1164.all;

ENTITY tu3_2 IS
    port(
        a, b,c,d : in std_logic;
        Sel: in std_logic_vector (1 downto 0);
        f : out std_logic);
END ENTITY;

ARCHITECTURE behave OF tu3_2 IS
BEGIN
    process (a, b,c,d,sel)
    begin
        Case sel is
            When "00" =>
                f <= a;
            When "01" =>
                f <= b;
            When "10" =>
                f <= c;
            When "11" =>
                f <= d;
        End case;
    End process;
End architecture;
```

 simulation mood: functional

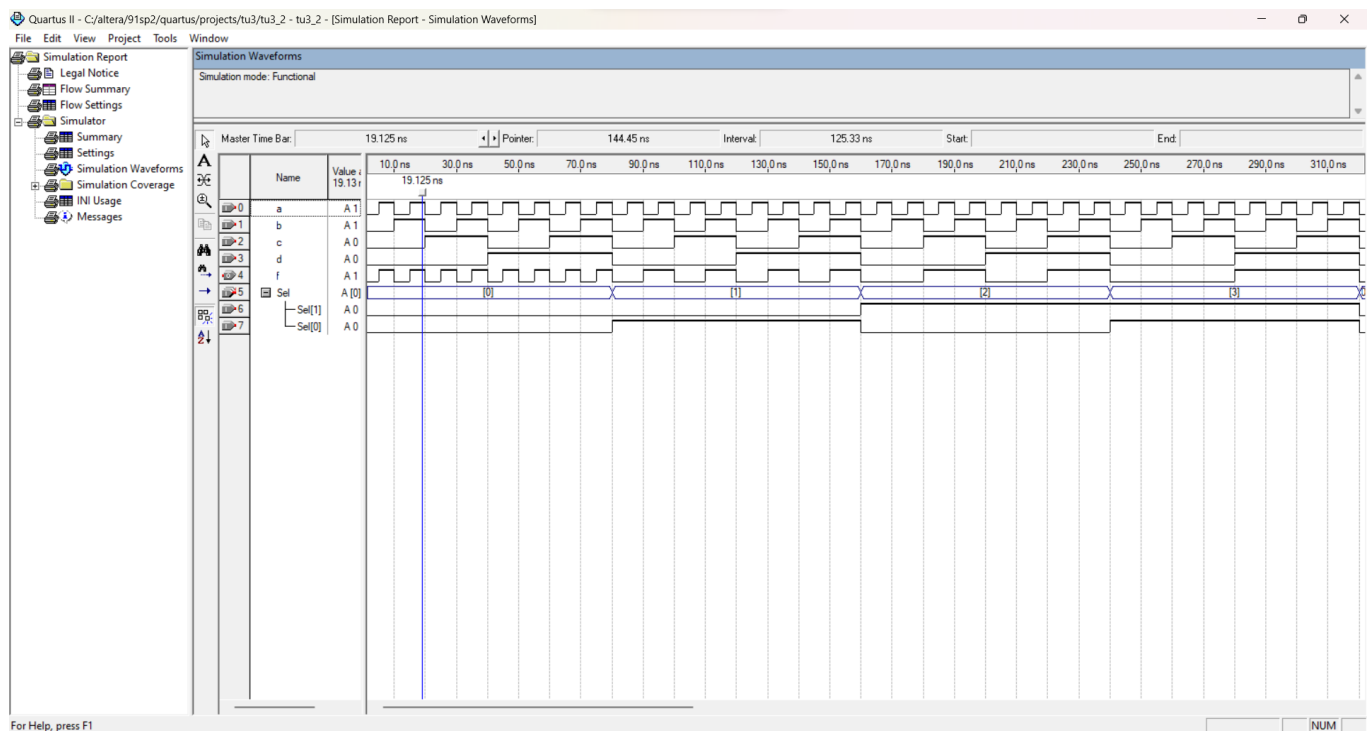

the output **F** depends on the selection line:
 when the selection lines values were both zeros "00"
 the output was same as the input **A**.
 and the values "01" gives the output same as **B**.
 "10" gives **C**.
 "11" gives **D**.