

Tutorial 2

Name: Nour-alдин Ibrahim Ahmed Elbadawy

ID: 2018-13394

Sheet 2


Q2:

write the behavioral VHDL code

```
library ieee;
use ieee.std_logic_1164.all;

entity tutorial2 is
port(
    x,y,z: in std_logic;
    F: out std_logic);
end tutorial2;

 architecture behave of tutorial2 is
    signal sig1, sig2: std_logic;
begin
    sig2 <= not(z);
    sig1 <= sig2 when (y = '1') else '0';
    F <= sig2 when (x='1') else sig1;
end behave;
```




Q3:

```
library ieee;
use ieee.std_logic_1164.all;


entity tutorial2 is
port(
    control, sel: in std_logic;
    A,B : out std_logic);
end tutorial2;

architecture behave of tutorial2 is
signal X1, X2, X3, X4: std_logic;
begin
X1 <= control and sel;
X2 <= sel and (not(control));
X3 <= X4 when(X1='1') else 'Z';
X4 <= X3 when(X2='1') else 'Z';
A <= X4;
B <= X3;
end behave;
```

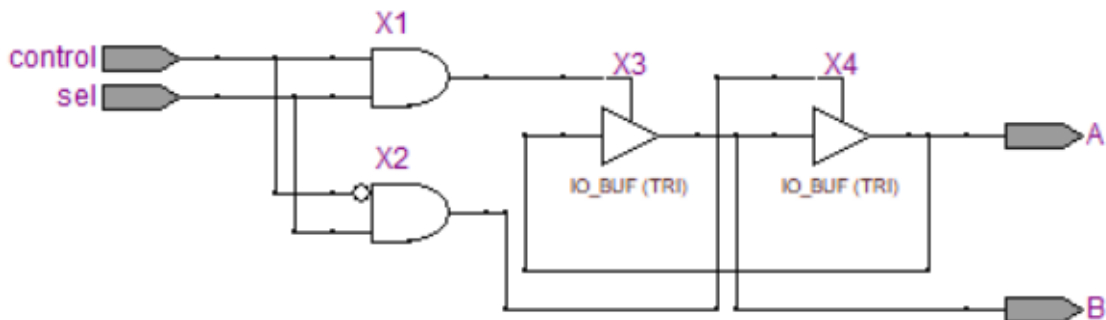

Sheet 1

Q5

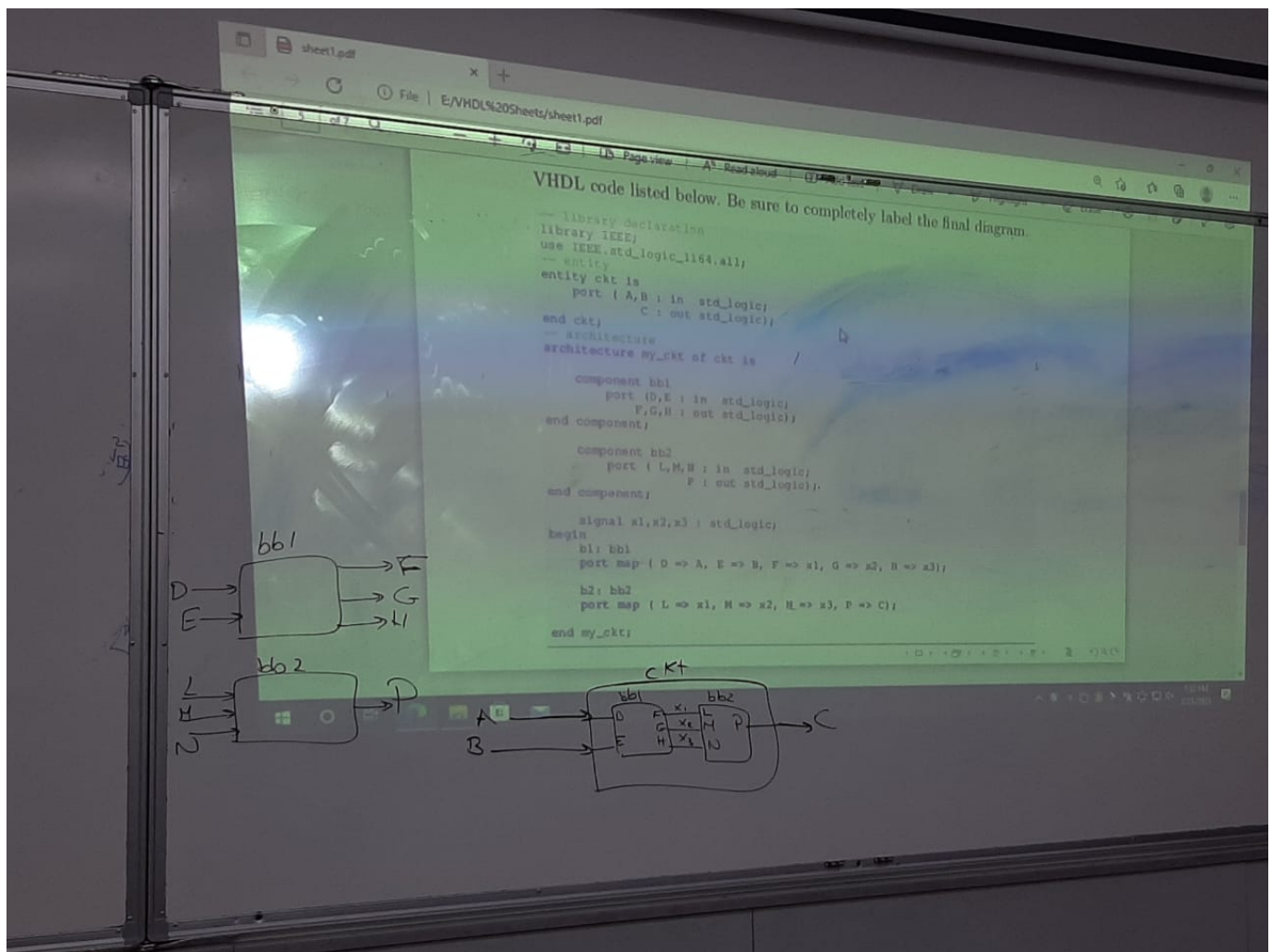

Q6


```

library ieee;
use ieee.std_logic_1164.all;

entity mux1 is
  port(
    A,B: in std_logic_vector(7 downto 0);
    sel: in std_logic;
    Y: out std_logic_vector(7 downto 0) );
end mux1;

architecture behave of mux1 is
begin
  Y <= A when(sel = '1') else B;
end behave;

```

 


```

library ieee;
use ieee.std_logic_1164.all;

entity reg1 is
port(
    x : in std_logic_vector(7 downto 0);
    lda,clk : in std_logic;
    f : out std_logic_vector(7 downto 0) );
end reg1;

architecture behave of reg1 is
begin
    process (clk,lda)
    begin
        if ( rising_edge (clk) ) then
            if(lda = '1') then
                f <= x;
            end if;
        end if;
    end process;
end behave;

```

 

```

library ieee;
use ieee.std_logic_1164.all;

entity tutorial2 is
port(
    lda,clk,sel: in std_logic;
    A,B: in std_logic_vector(7 downto 0);

    f: out std_logic_vector(7 downto 0)
);

end tutorial2;

architecture behave of tutorial2 is

signal x1: std_logic_vector(7 downto 0);

component mux1 is
port(
    A,B: in std_logic_vector(7 downto 0);
    sel: in std_logic;
    Y: out std_logic_vector(7 downto 0)
);
end component;

component reg1 is
port(
    x : in std_logic_vector(7 downto 0);
    lda,clk : in std_logic;
    f : out std_logic_vector(7 downto 0)

```

```

);
end component;

begin

u1: mux1 port map( A => A, B => B, sel => sel, y => x1);
u2: reg1 port map( lda => lda, clk => clk, x => x1, f => f);

end behave;

```

