

# Assignment 3

Name: Nour-alдин Ibrahim Ahmed Elbadawy

ID: 2018-13394


## Main Code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;


entity lec5 is
port(
    x,y : in integer range 0 to 2;

    z : out integer range 0 to 4;
    sel : in std_logic
    );
end lec5;
architecture behave of lec5 is
begin
    process (x,y,sel)
        begin
            if(sel = '1') then z <= x+y;
            else z<= x-y;
            end if;
        end process;
    end behave;
```

# RTL

 

## Waveform Simulation

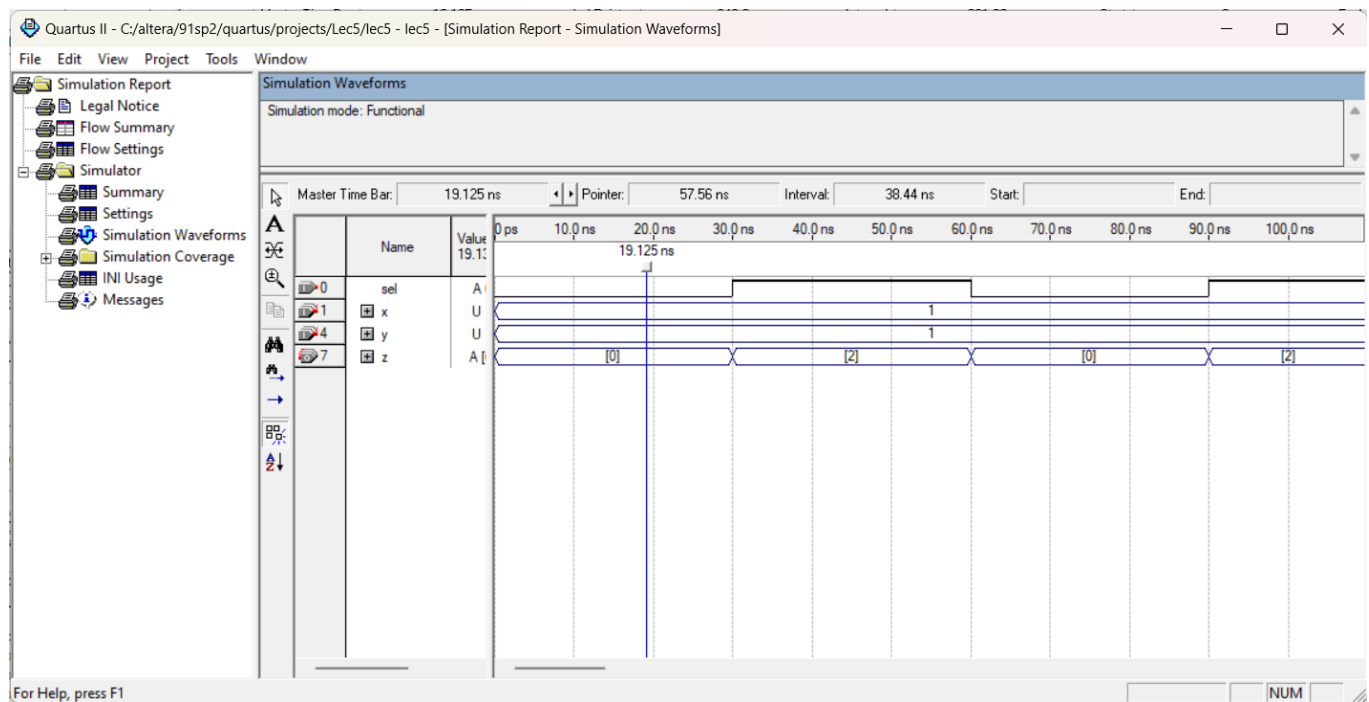

## Analysis

when the selection line = 0, multiplexer select the subtraction as Output  
while in case that selection line = 1, multiplexer select the Addition as Output  
and this shown in the waveform simulation above